

## Lab 2 Pre-lab

**Due Date** : 14/10/2019, 12:30

**Name** : Mesut Selim Serbes


**No** : 2017510100

**Group** : (e.g. Monday 14:00, 5)

**Subject**: Thevenin Equivalent and Maximum Power Transfer


### Pre-lab Procedure:

- ➔ Each student must prepare and upload the pre-lab INDIVIDUALLY!
- ➔ Upload as a .PDF file.

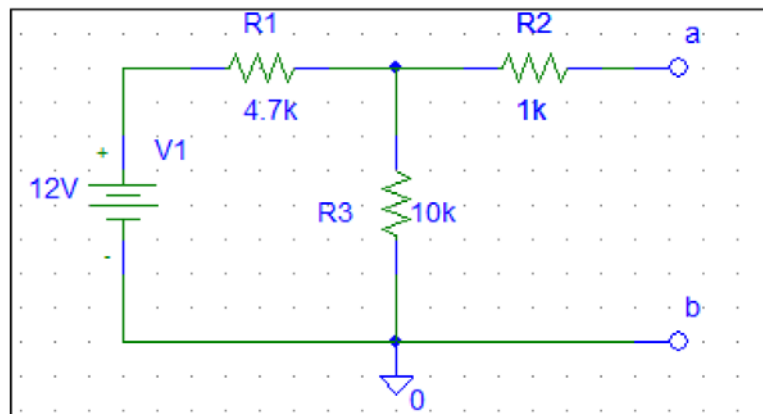

**Figure 1**

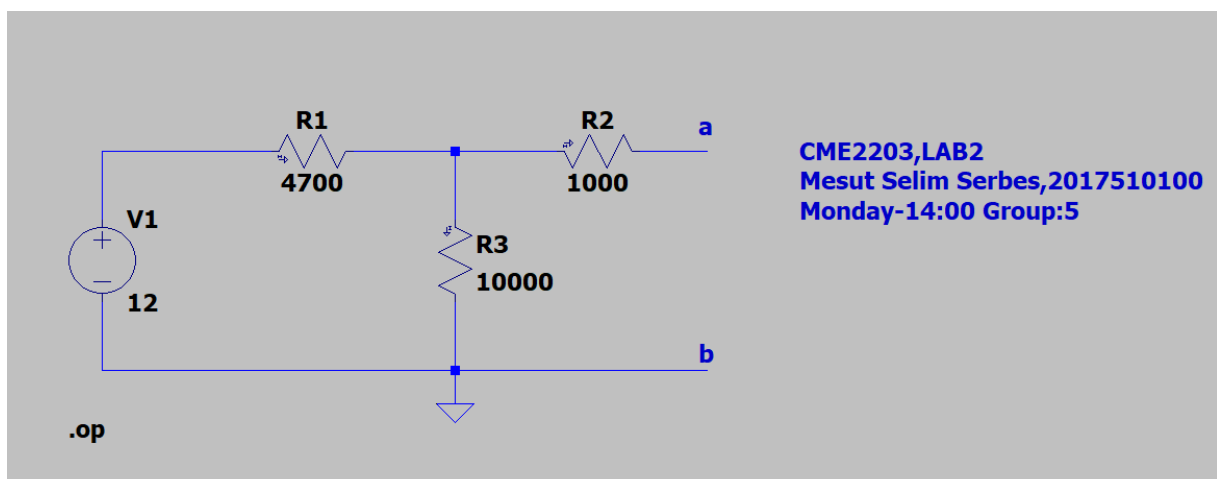1. Which colors represent the resistors used in the circuit? (ex. Violet, Yellow, Brown)  
Ignore the tolerances for now.
  - a.  $4.7\text{K}\Omega$  : Yellow, Violet, Red
  - b.  $1\text{K}\Omega$  : Brown, Black, Red
  - c.  $10\text{K}\Omega$  : Brown, Black, Orange
2. Draw the schematic for the circuit in Figure 1 using LTSpice and simulate it.



Also, remember to label the points a and b. Save your schematic. Run a DC operation analysis and note the open circuit voltage across a and b (You should determine the node that corresponds to a-b in the circuit).  $V_{oc} = 8.16327V$ .

- Now, connect the points a and b with a wire. Note that now R2 has some current flowing through it and it's the same current flowing through a-b, so  $I_{ab}=I_{sc}=I_2= 1.94489 \text{ mA}$ .
- We have everything we need to calculate the Thevenin Resistance of the circuit because  $R_{Th}=V_{oc}/I_{sc}=8.16327/1.94489 \text{ m}=4.19729136K\Omega$


(Interesting: if we wanted to find the equivalent resistance in the circuit, we have  $R1||R3+R2 = [R1R3/(R1+R3)]+R2 = 4.19727891K\Omega$ ).

- Replace the wire between a and b with a  $1K\Omega$  resistor and name it  $R_{load}$ . Run a DC operation analysis. Use this result to fill in the table below up to 3 decimal digits (ex. 1.227). You should change the resistor value to fill values for each row. Note that  $I_{ab} = I_{load}$  and  $V_{ab}$  corresponds to the node at the top of  $R_{load}$ . Then use your calculator to find the power at  $R_{load}$  by multiplying  $I_{ab}$  and  $V_{ab}$  and fill in the table values.


Load	Iab (mA)	Vab (V)	Pab=IabxVab (mW)
1K $\Omega$	1.570	1.570	2.464
2K $\Omega$	1.317	2.634	3.468
3K $\Omega$	1.134	3.402	3.857
4K $\Omega$	0.995	3.983	3.963
5K $\Omega$	0.887	4.437	3.935
6K $\Omega$	0.800	4.803	3.842
7K $\Omega$	0.729	5.103	3.720
8K $\Omega$	0.669	5.354	3.581
9K $\Omega$	0.618	5.567	3.440
10K $\Omega$	0.574	5.749	3.299

- Draw current, voltage and power values for each step of  $R_{load}$ . You can use MS Excel or MATLAB/Octave but you must include the graph in this document. When is the power maximum?

MAX CURRENT

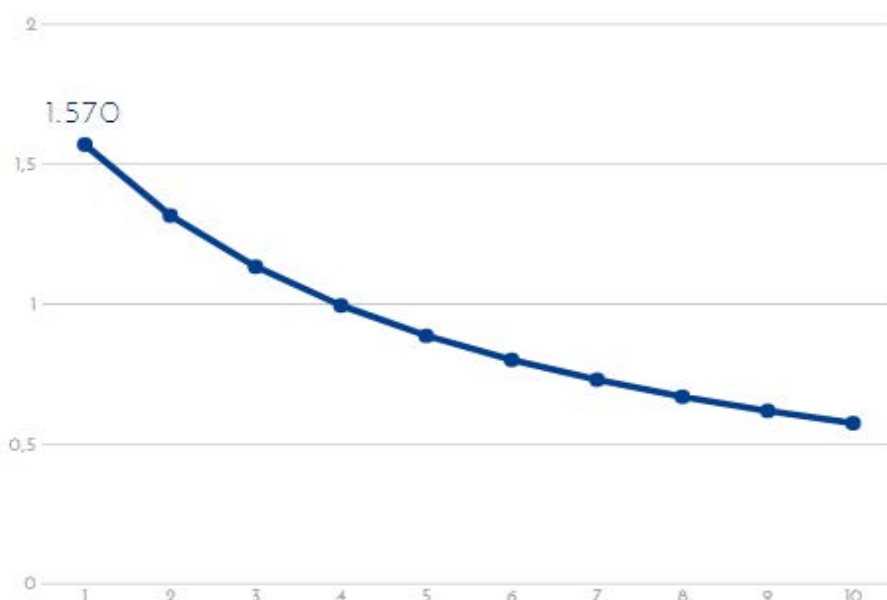

MAX VOLTAGE

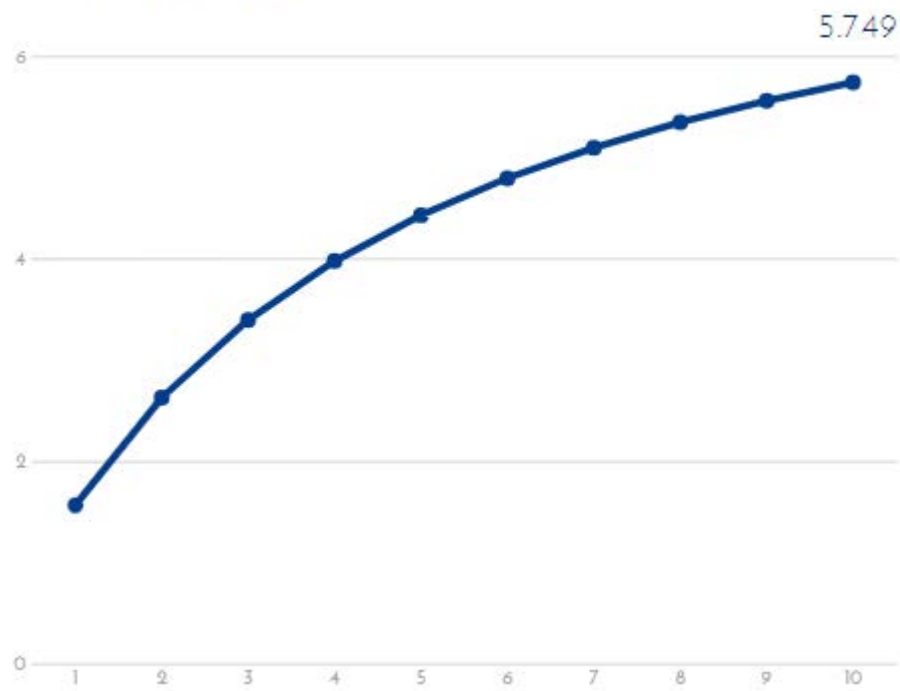

MAX POWER

