

CME 2203 Lab 4 Pre-lab

Due Date: 4 November 2019, 12:30


Name: Mesut Selim SERBES

Student Number: 2017510100

Session- Group: (e.g. Monday 14:00, 5)

Subject: Diodes

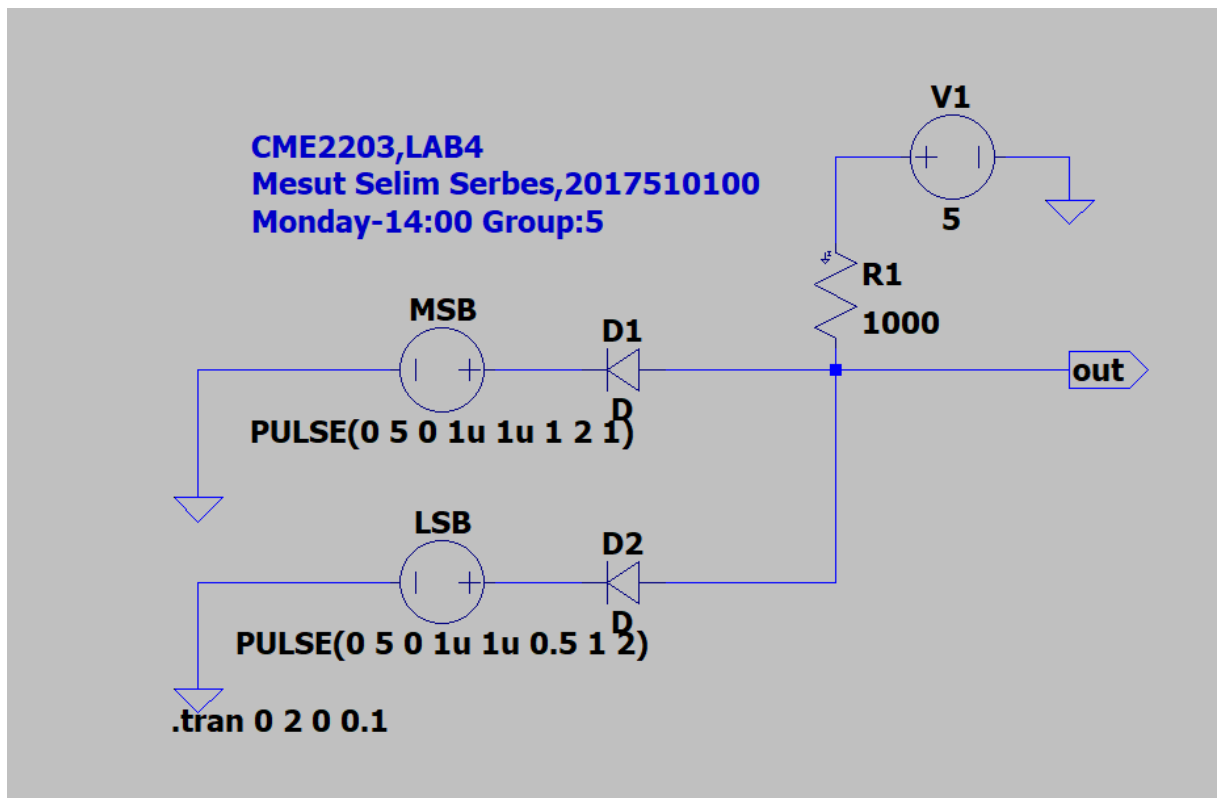Draw the following circuit on LTSpice Schematics and save to a folder of your choice. Note that the screenshot we want is more than just the circuit; we want simulation graphs as well.



1. For your screenshot, top of the window should contain the graph plot panes, and the bottom of the window should contain:
 - a. The circuit diagram
 - b. The text label
2. Create the circuit schematic shown above. Note that we use **square pulses** to create all combinations of MSB and LSB. You can see the parameter values below the logic input voltage sources MSB and LSB. You can make both MSB and LSB provide **pulses for 4 cycles**.
3. Adjust the component values as follows:
 - a. For V1 we can just assign a DC value of +5V.
 - b. We want MSB and LSB to act as a switch we open and close periodically, so we want it to produce a square wave voltage pattern.
 - c. To achieve this, right click on LSB and click Advanced. Select PULSE. Enter the parameters as follows (letter **u** works for microsecond):


- i. $V_{\text{initial}}(\text{V})$: 0
- ii. $V_{\text{on}}(\text{V})$: 5
- iii. $T_{\text{delay}}(\text{s})$: 0
- iv. $T_{\text{rise}}(\mu\text{s})$: 1u
- v. $T_{\text{fall}}(\mu\text{s})$: 1u
- vi. $T_{\text{on}}(\text{s})$: 0.5
- vii. $T_{\text{period}}(\text{s})$: 1
- viii. N_{cycles} : 2

This setting creates a square wave with a period of 1s, and because it's on(+5V) at only 0.5s, so its DUTY CYCLE is 50%. It lasts for 2 cycles, so for (cycle no)x(period T) = 2x1 = 2 seconds.

- d. Now, right click on MSB and click Advanced. Select PULSE. Enter the parameters as follows (letter **u** works for microsecond):

- i. $V_{\text{initial}}(\text{V})$: 0
- ii. $V_{\text{on}}(\text{V})$: 5
- iii. $T_{\text{delay}}(\text{s})$: 0
- iv. $T_{\text{rise}}(\mu\text{s})$: 1u
- v. $T_{\text{fall}}(\mu\text{s})$: 1u
- vi. $T_{\text{on}}(\text{s})$: 1
- vii. $T_{\text{period}}(\text{s})$: 2
- viii. N_{cycles} : 1

This setting creates a square wave with a period of 2s. It lasts for only one cycle, so 1x2 = 2 s.

- 4. Now, we are ready to run the simulation! Click on the running man  and edit the simulation command (Remember, you can also change this command later by going to Simulate\Edit Simulation Command):

- a. Under the Transient tab, select the following parameters:
 - i. Stop Time : 2
 - ii. Time to Start Saving Data : 0
 - iii. Maximum Time Step : 0.1 and click OK.

This means you run the simulation from 0 to 2s. with time intervals of 100ms. Click the running man again. You should see an empty graph on top of the window now. Let's fill it with graphs!

- b. Now, move the cursor to the graph, right click and select Add Plot Pane. Now you should have a total of three voltage plot panes.
- c. Click on the top graph pane, then click the **red probe** appearing on the circuit to the wire connecting to positive side of LSB, to the left of diode. This is our first logic input.

- d. Click on the middle graph pane, then click the **red probe** appearing on the circuit to the wire connecting to positive side of MSB, to the left of diode. This is our second logic input.
- e. Click on the bottom graph pane, then click on the wire that connects to **Out** port. This is the logic output.

So your final screenshot should be like this (Out voltage not shown)

